

NAME:- YASHRAJ. V. AWARE

ROLL NO:- 2244006

BATCH :- D-1

Page No.	1
Date	

ASSIGNMENT:- 02

AIM:-

To realise full adder and full subtractor using a) Basic gates and b) NA Universal gates.

I.C REQUIRED:-

IC 7486,
(XOR)

IC 7408,
(AND)

IC 7432,
(OR)

IC 7400,
(NAND)


PROCEDURE :-

The following operations could be performed by writing down pin diagrams, Truth Table, K-maps, and expressions of full adder and full subtractor.


THEORY :-

- ① The full adder performs addition of two binary digits A and B together with a "carry-in" from a previous addition.
- ② A full adder has three inputs A, B and "CARRY-IN" which is abbreviated here as 'in' and two output, 'sum' and 'carry out'.
- ③ The full subtractor performs subtraction between two binary digits A and B with an extra "borrow" from previous subtraction.
- ④ A full subtractor has three inputs A, B and "BORROW" and two output.


PIN DIAGRAM:-

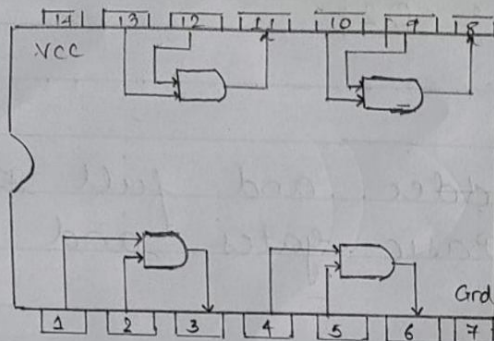


IC 7408 (AND GATE)

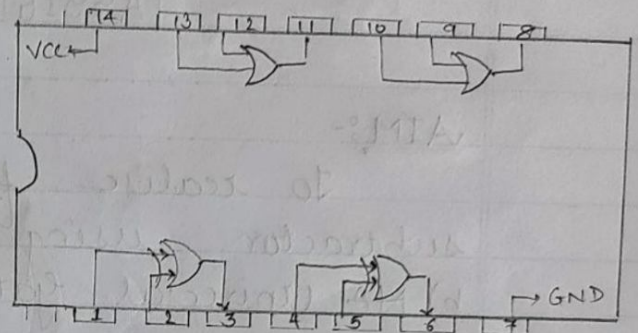

IC 7432 (OR GATE)

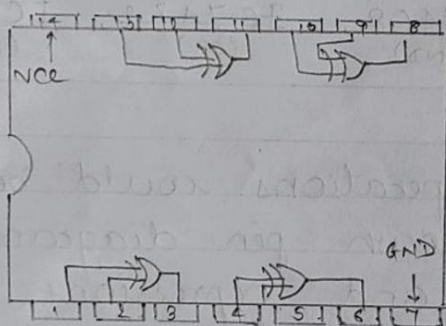

IC 7486 (XOR GATE)

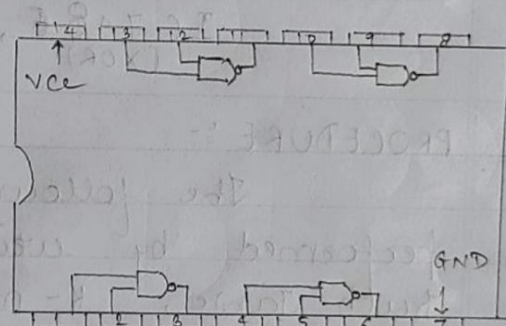

IC 7400 (NAND GATE)

⑤ Full adder truth table

INPUT			OUTPUT	
A	B	Cin	Sum	Count
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

⑥ Full subtractor truth table

INPUT			OUTPUT	
A	B	Bin	Diff.	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


a) FULL ADDER USING BASIC GATES AND UNIVERSAL GATES

① K-MAP for sum:-


sum AB	00	01	11	10
Cin				
0	0	1	0	1
1	1	0	1	0

$$\text{Sum} = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + ABC_{in} + A\bar{B}\bar{C}_{in}$$

FULL ADDER THROUGH BASIC GATES

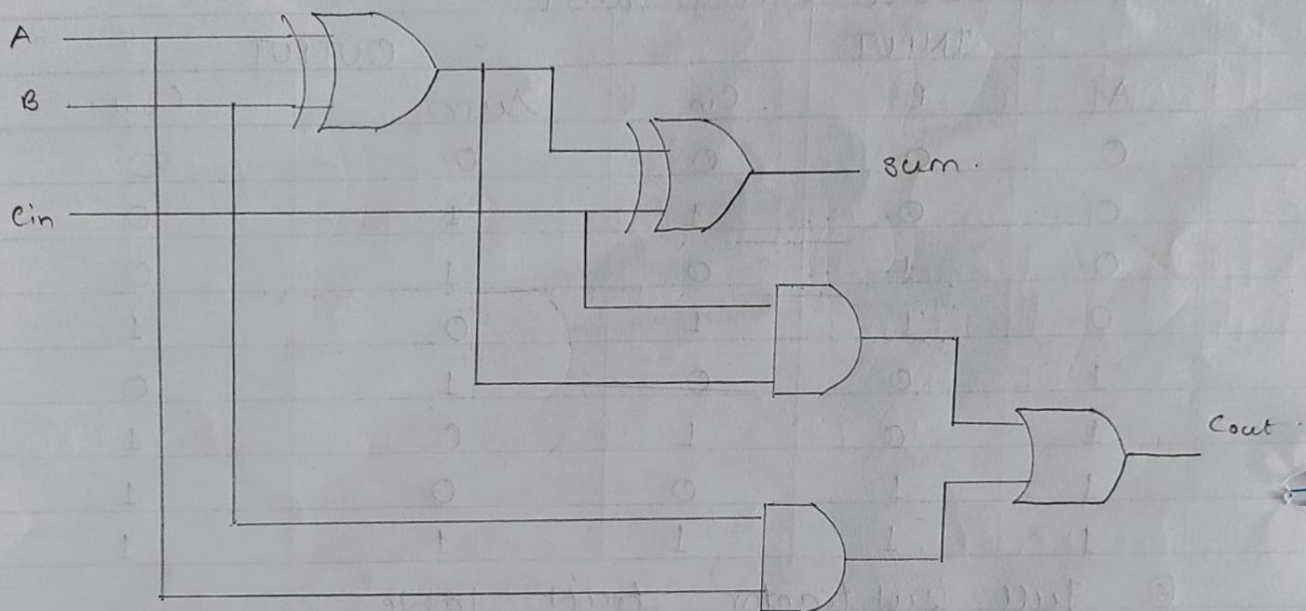

FULL ADDER USING NAND GATES:-

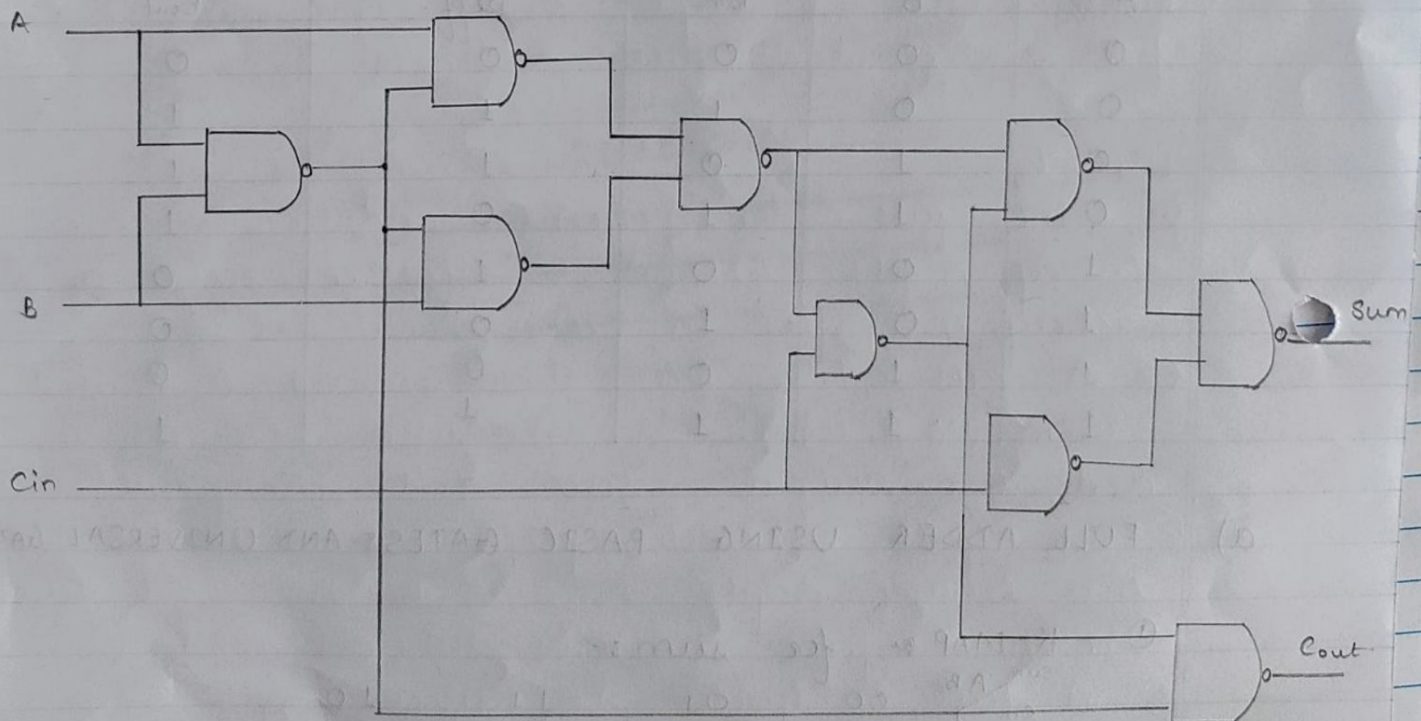

$$\begin{aligned}
 \text{Sum} &= \text{cin} (\bar{A}\bar{B} + AB) + \bar{\text{cin}} (\bar{A}B + \bar{B}A) \\
 &= \text{cin} + \bar{\text{cin}} (A \oplus B) \\
 &= \text{cin} \oplus (A \oplus B)
 \end{aligned}$$

② K-MAP for Cout :-

	AB	00	01	11	10
Cin					
0		0	0	1	0
1		0	1	1	1

$$\begin{aligned}
 \text{Cout} &= AB + AC_{in} + BC_{in} (A + \bar{A}) \\
 &= \bar{A}BC_{in} + A\bar{B}C_{in} + ABC_{in} + ABC_{in} \\
 &= AB + C_{in} (\bar{A}B + AB) \\
 &= AB + C_{in} (A \oplus B)
 \end{aligned}$$

b) FULL SUBTRACTOR USING BASIC GATES AND UNIVERSAL GATES:

a) K-MAP FOR DIFFERENCE


	diff: B Bin	00	01	11	10
A					
0		0	1	0	1
1		1	0	1	0

$$\begin{aligned}
 \text{Diff} &= \bar{A}\bar{B}B_{in} + A\bar{B}B_{in} + \bar{A}BB_{in} + AB B_{in} \\
 &= B_{in} (\bar{A}\bar{B} + AB) + \bar{B}_{in} (A\bar{B} + \bar{A}B) \\
 &= B_{in} (A \oplus B) + \bar{B}_{in} (A \oplus B) \\
 &= \overline{B_{in} (A \oplus B)} + \bar{B}_{in} (A \oplus B) \\
 &= B_{in} \oplus (A \oplus B)
 \end{aligned}$$

b) K-MAP FOR Bout :-

	Bout B Bin	00	01	11	10
A					
0		0	1	1	1
1		0	0	1	0

FULL SUBTRACTOR THROUGH BASIC GATES:-

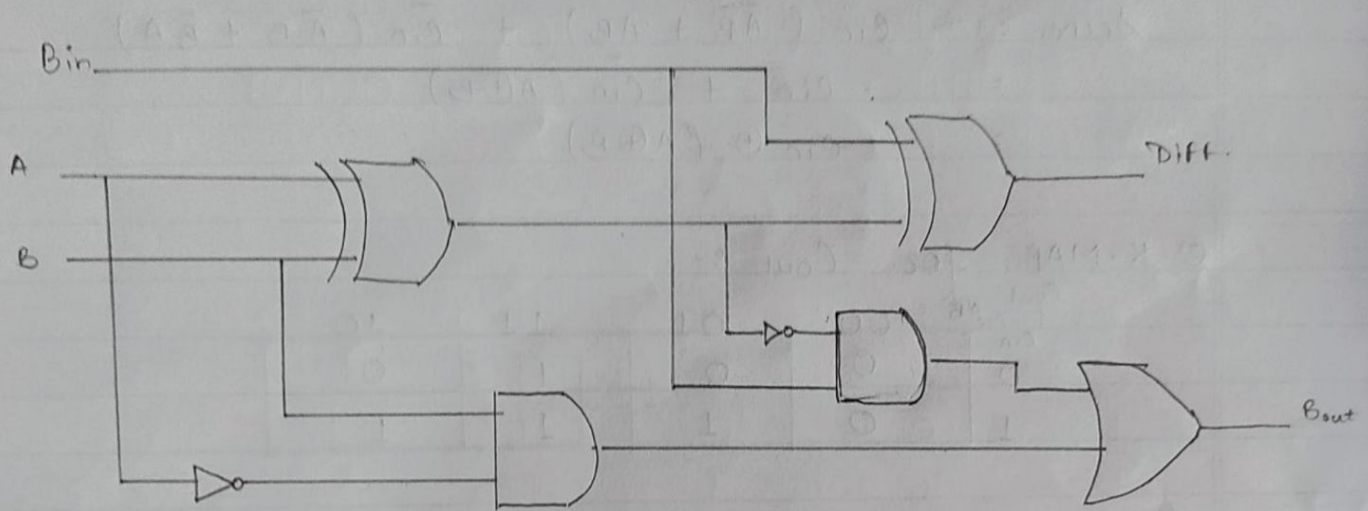

$$\begin{aligned}
 B_{out} &= \bar{A}\bar{B}Bin + \bar{A}B\bar{B}in + \bar{A}BBin + AB\bar{B}in \\
 &= \bar{A}Bin(B + \bar{B}) + \bar{A}B(Bin + \bar{B}in) + BBin(A + \bar{A}) \\
 &= \bar{A}Bin + \bar{A}B + BBin
 \end{aligned}$$

CONCLUSION:-

By following above procedures, truth tables, k-maps and expressions we were able to derive desired results.