

NAME:- YASHRAJ. V. AWARE

ROLL NO:- 2244006

BATCH :- D1

PRN :- 22110167

Page No.	1
Date	

### ASSIGNMENT:- 03.

#### AIM:-

Design and implement code which converts  
a) Binary to gray code and  
b) BCD to excess 3.

#### I.C REQUIRED:-

I.C 7486 (XOR), IC 7408 (AND)


I.C 7432 (OR), IC 7404 (NOT) and toolkit.

#### THEORY:-


- ① Binary coded decimal (BCD), in this each decimal digit is represented by 4-bit binary numbers.
- ② The 4-bit representation of decimals is done of numbers (0000 to 1111)
- ③ This representation is done for only first ten decimals i.e (0-9).
- ④ Excess-3 binary code is an unweighted self-complementary BCD code.
- ⑤ Self-complementary property means that the 1's complement of an excess-3 number is the excess-3 code of nine's complement of corresponding decimal number.
- ⑥ This property is useful since a decimal number can be nine's complemented (for subtraction) as easily as binary ones can be ones' complementing, just by inverting all the bits.




## PIN DIAGRAM:-

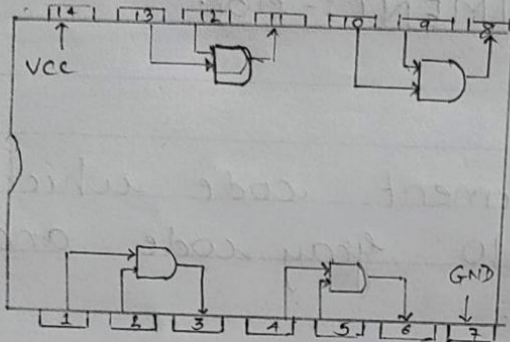


IC 7408 (AND GATE)

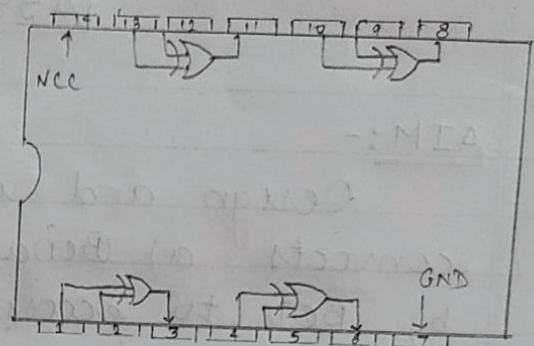

IC 7486 (XOR GATE)

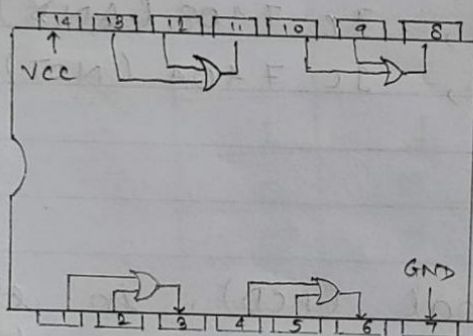

IC 7432 (OR GATE)

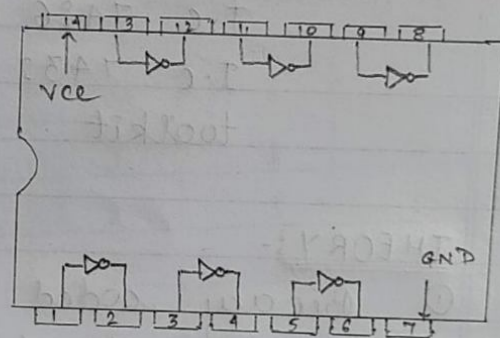

IC 7404 (NOT GATE)



a) Binary to Gray conversion:-

BINARY CODE				GRAY CODE			
$B_3$	$B_2$	$B_1$	$B_0$	$G_3$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

① FOR  $G_3$  :-

$B_3 \backslash B_2$	00	01	10	11
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

expression :  $G_3 = B_3 \bar{B}_2 + B_3 B_2$

$G_3 = B_3 (\bar{B}_2 + B_2)$

$G_3 = B_3$

Binary to Gray code :


expressions :

①  $G_3 = B_3$

②  $G_2 = B_3 \oplus B_2$

③  $G_1 = B_1 \oplus B_2$

④  $G_0 = B_1 \oplus B_0$

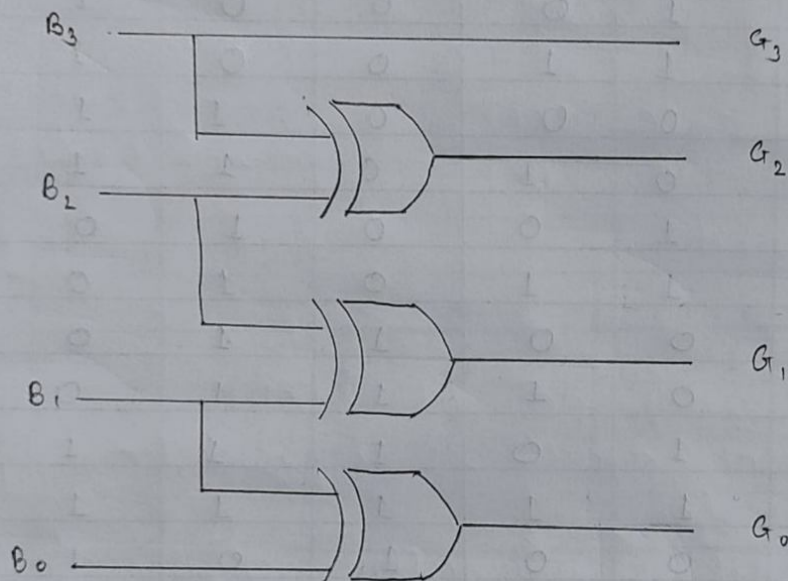



② FOR  $G_2$  :-

$B_3 B_2$	00	01	11	10
$B_3 B_0$				
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

expression :  $G_2 = \bar{B}_3 B_2 + B_3 \bar{B}_2$   
 $G_2 = B_3 \oplus B_2$

③ FOR  $G_1$  :-

$B_3 B_2$	00	01	11	10
$B_1 B_0$				
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	1

expression :-  $G_1 = B_1 \bar{B}_2 + \bar{B}_1 B_2$   
 $G_1 = B_1 \oplus B_2$


④ FOR  $G_0$  :-

$B_3 B_2$	00	01	11	10
$B_1 B_0$				
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

expression :-  $G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0$   
 $G_0 = B_1 \oplus B_0$

Bcd to Excess-3 :-  
expression :-

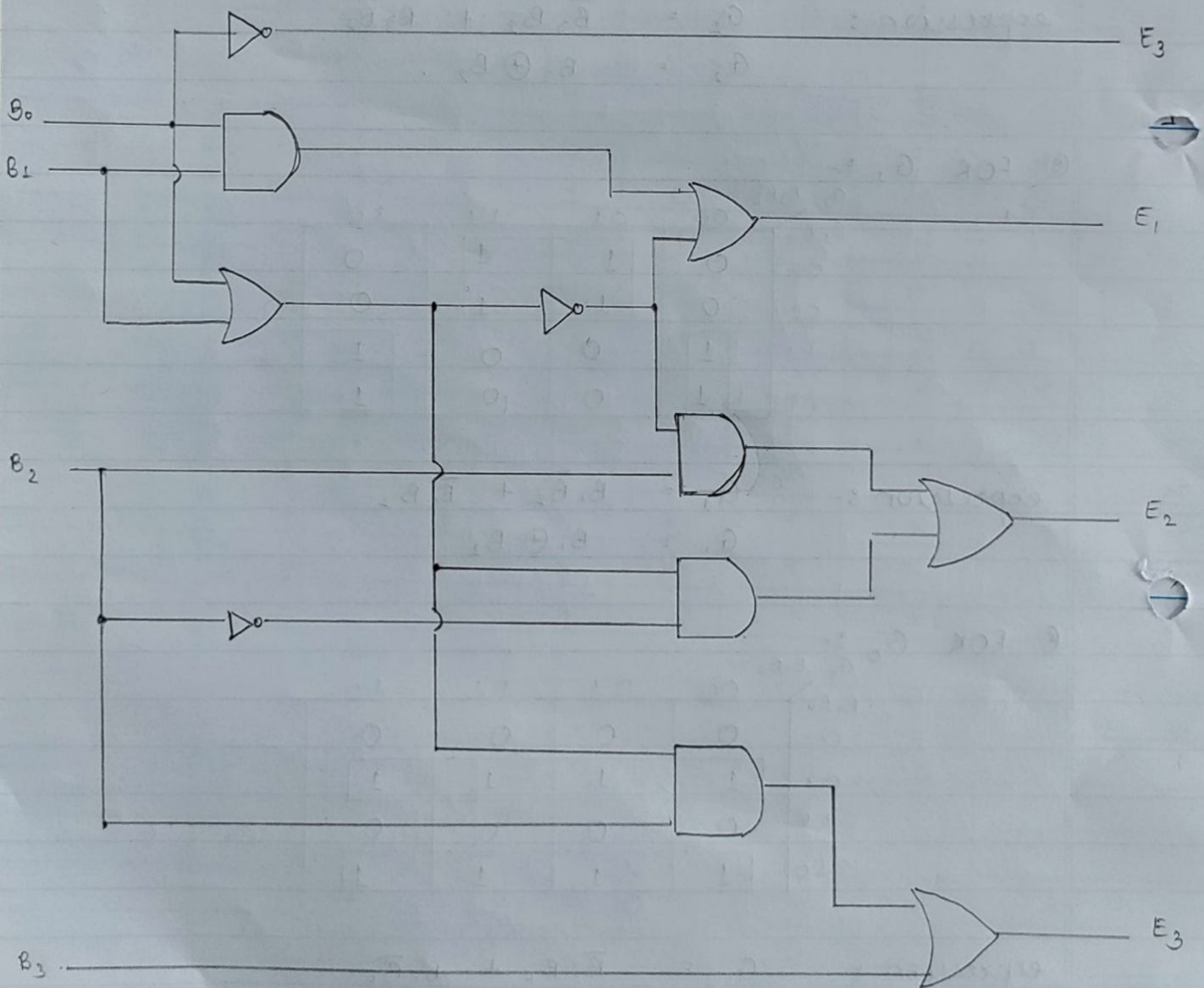- ①  $E_3 = \bar{B}_0$
- ②  $E_2 = \bar{B}_2 B_1 + \bar{B}_2 B_0 + B_2 \bar{B}_1 \bar{B}_0$
- ③  $E_1 = B_1 B_0 + \bar{B}_1 \bar{B}_0$
- ④  $E_0 = B_3 + B_2 B_1 + B_2 B_0$





b) BCD to excess-3:-

BINARY CODE				EXCESS-3 GRAY CODE			
$B_3$	$B_2$	$B_1$	$B_0$	$E_3$	$E_2$	$E_1$	$E_0$
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

① FOR  $E_3$ :-

$E_3$ $B_3 B_2$	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

expression :  $E_3 = \overline{B_0}$



② FOR  $E_2$  :-

$E_2 \ B_3 B_2$	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

expression :-  $E_2 = \bar{B}_2 B_1 + \bar{B}_2 B_0 + B_2 \bar{B}_1 \bar{B}_0$

③ FOR  $E_1$  :-

$E_1 \ B_3 B_2$	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

expression :-  $E_1 = B_1 B_0 + \bar{B}_1 \bar{B}_0$

④ FOR  $E_0$  :-

$E_0 \ B_3 B_2$	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

expression :-  $E_0 = B_3 + B_2 B_1 + B_2 B_0$

CONCLUSION :-

The circuit of above conversion was successfully executed, and by going through the above truth table, K-maps and expressions.