

ASSIGNMENT :- 04

AIM:-

To design and realise BCD adder using 4-bit binary adder.


I.C REQUIRED:-

I.C. 7483 (4-bit binary full adder)

THEORY:-

- ① A BCD adder adds two BCD digits and produces a BCD digit number which cannot be greater than 9.
- ② Two given BCD numbers are to be added using rules of binary addition, if sum is less than or equals to 9 and carry is equal to 0, then correction is not necessary and the sum is in true BCD form.
- ③ But if sum is invalid BCD or carry is generated then the result requires correction.
- ④ The result can be corrected by adding 6 (0110) to it.
- ⑤ The 4 bit binary adder IC 7483 can be used to perform addition of BCD numbers.
- ⑥ In this if 4-bit output is not valid, then the BCD adder is cascaded to add the numbers several digits long by connecting carry-in of a stage to carry-out of another stage.

PIN DIAGRAM:-

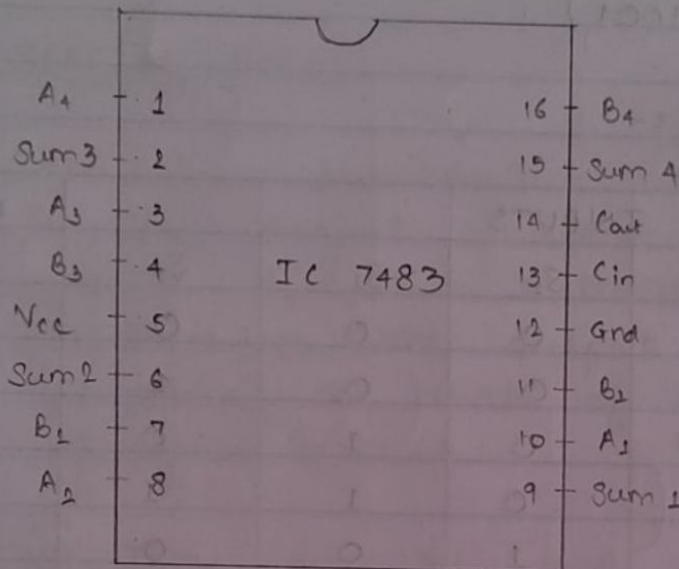

⑦ The output of combinational circuit should be 1 if sum produced by adder is greater than 9 (1001).


a) TRUTH TABLE:-

Decimal	INPUTS				OUTPUT Y
	S_3	S_2	S_1	S_0	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

b) K-MAPS:-

$S_3 S_2$ \ $S_1 S_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

CIRCUIT DIAGRAM

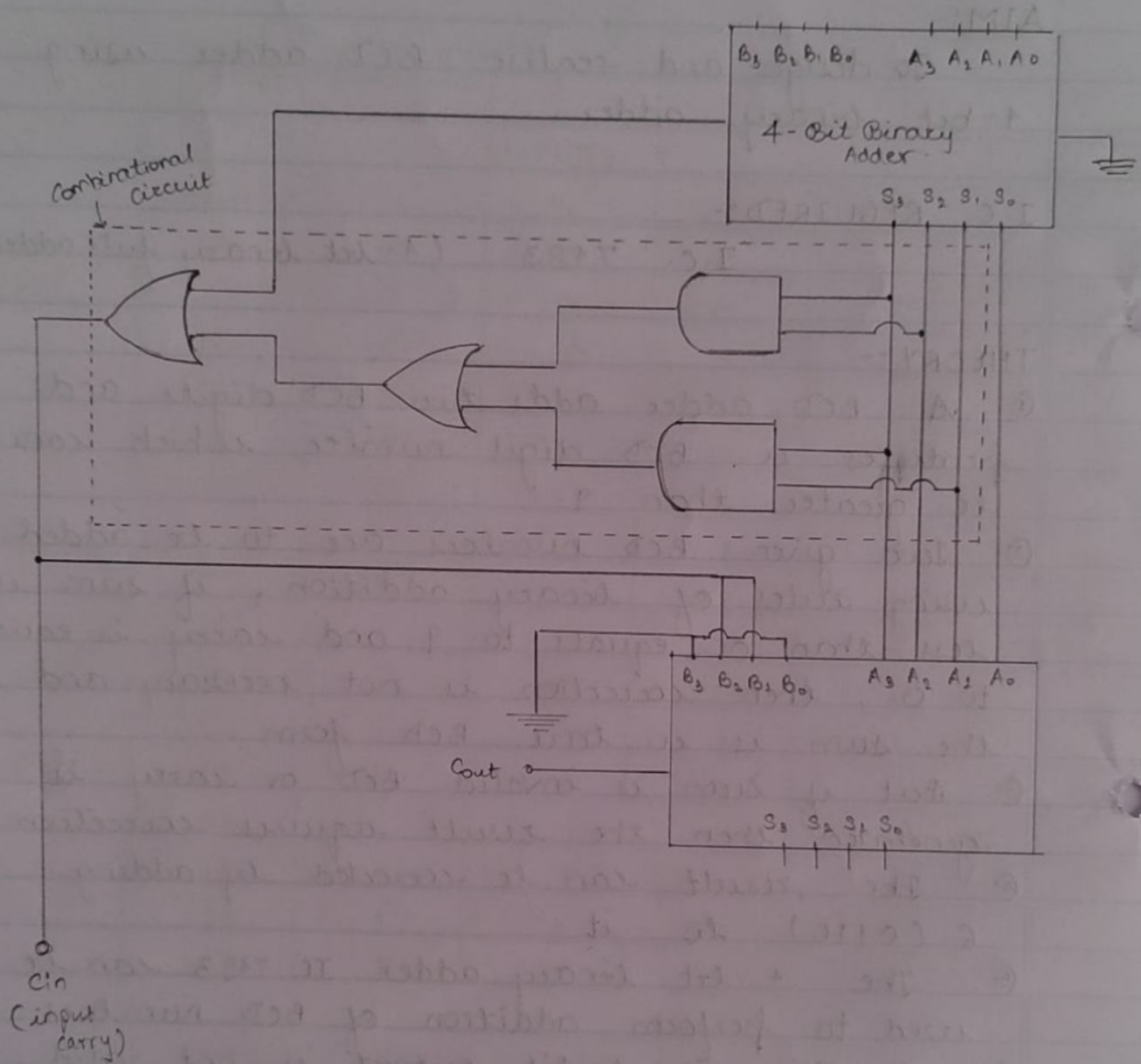

$$Y = S_3 S_2 + S_3 S_1$$

$$Y = S_3 (S_2 + S_1)$$

c) SPECIAL CASES:-

CASE I :- sum ≤ 9 and carry = 0

- ① The output of combinational circuit $Y=0$ hence $B_3 B_2 B_1 B_0 = 0000$ for binary adder
- ② Therefore the output of adder circuit-2 is same as that of adder-1 i.e. sum of first circuit.

CASE II :- sum > 9 and carry = 0

- ① If $S_3 S_2 S_1 S_0$ of adder-1 (sum-1) is greater than 9 then output of combinational circuit becomes 1.
- ② $B_3 B_2 B_1 B_0$ will be equal to 0110 (of adder 2) hence six will be added to sum output of adder 1

CASE III :- sum > 9 and carry = 1

- ① carry output of adder 1 is high and $Y=1$ $B_3 B_2 B_1 B_0 = 0110$ (of adder 2). Six will be added to sum of output of adder 2

CONCLUSION:-

The 4 bit BCD adder has been verified by using IC 7483. This is done with the help of simplified equations and K-maps.